

Discover more

K-Map practice problems

Computer science textbook

maps

Karnaugh Map

Number of Variables:

4 Variables

Clear All

Fill All with 1

CD
AB

00011110

10

1

0

1

0

1

3

2

01

1

0

1

11

0

0

0

10

1

0

1

Click cells to toggle values: 0 → 1 → X → 0

X represents "don't care" condition (can be either 0 or 1)

Simplified K-Map Result

SOP Form

POS Form

CD
AB

00011110

10

1

0

1

0

1

3

2

01

1

0

1

11

0

0

0

10

1

0

1

Simplified Boolean Expression

A'D' + B'D' + C'

Original Groups

Original

A'B'C'D' + A'B'CD' + A'BC'D' + A'BCD'

Minterms

(0, 2, 4, 6)

Simplified

A'D'

Original

A'B'C'D' + A'B'CD' + AB'C'D' + AB'CD'

Minterms

(0, 2, 8, 10)

Simplified

B'D'

Original

A'B'C'D' + A'B'C'D + A'BC'D' + A'BC'D + AB'C'D' + AB'C'D + ABC'D' + ABC'D

Minterms

(0, 1, 4, 5, 8, 9, 12, 13)

Simplified

C'

Logic Circuit

Truth Table

#	A	B	C	D	Output		
0	0	0	0	0	0	1	X
1	0	0	0	1	0	1	X
2	0	0	1	0	0	1	X
3	0	0	1	1	0	1	X
4	0	1	0	0	0	1	X
5	0	1	0	1	0	1	X
6	0	1	1	0	0	1	X
7	0	1	1	1	0	1	X
8	1	0	0	0	0	1	X
9	1	0	0	1	0	1	X
10	1	0	1	0	0	1	X
11	1	0	1	1	0	1	X
12	1	1	0	0	0	1	X
13	1	1	0	1	0	1	X
14	1	1	1	0	0	1	X
15	1	1	1	1	0	1	X

Click buttons to set output values:

0 or 1 or X

X represents "don't care" condition (can be either 0 or 1)

Minterms

Maxterms

© 2026 K-Map Solver. All rights reserved.

Visit us at: https://karnaughmapsolver.com